

# **EE-475L: Computer Architecture**



## **Lab Report**

### **Submitted by**

Ali Imran    2018-EE-62

### **Submitted to**

Mr. Umer Shahid

**Department of Electrical Engineering**

**University of Engineering and Technology, Lahore, Pakistan.**

## File Structure

We have the following file structure. All the tests are written in the `test.py` structure. Run the makefile to start the simulation. All the results are in the Figures directory.

```
├── ALU.sv
├── Branch_Condition.sv
├── Controller.sv
├── Data_Memory.sv
├── Figures
│   ├── ALU.png
│   ├── Branch.png
│   ├── ckt.png
│   ├── datamem.png
│   ├── gcd.png
│   ├── Immediate_Generator.png
│   ├── Instruction.png
│   ├── PC.png
│   └── Register.png
├── Immediate_Generator.sv
├── instruction_mem.mem
├── Instruction_Memory.sv
├── Makefile
├── Program_Counter.sv
├── Register_File.sv
├── Report.md
├── test.py
└── top.sv
```

## Single Cycle RISC-V Processor

For this project, we are going to implement a single cycle RISC-V processor as shown in figure below.

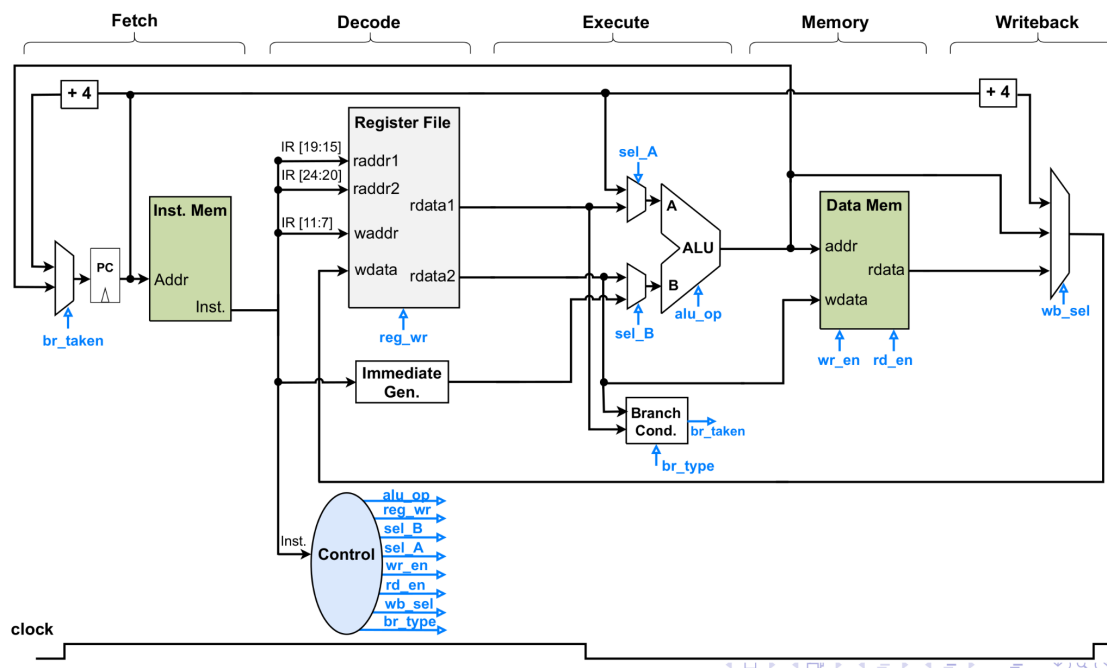


Figure 1. Datapath Implemented

For simulation, **cocotb** is used with **iverilog**. For testing the gcd code, the following assembly has been created.

```
addi a0,a0,15
addi a1,a1,30
addi a2,a2,0      #done=0
addi a3,a3,0      #constant =0
addi a4,a4,1      #msb_check=1
addi a5,a5,31
.loop:
  bne a2,a3,.abc   #while(done !=0)
  sub a7,a0,a1     #a-b
  srl a7,a7,a5     #checking msb
  xor a7,a7,a4     #checking if msb 1 or 0
  bne a7,a3,.else  #if true then a is not < b
  add a6,a3,a0     #temp=A
  add a0,a3,a1     #A=B
  add a1,a3,a6     #B=A
  beq a3,a3,.loop  #go back to loop
.else:
  bne a1,a3,.elseif #else if B !=0
  addi a2,a2,1     #else done=1
  beq a3,a3,.loop  #go back to loop
.elseif:
  sub a0,a0,a1     #A=A-B
  beq a3,a3,.loop  #go back to loop
.abc:
  add a7,a3,a0
  sw a7,0(x0)
  lw x18,0(x0)
```

*Listing 1. GCD RISC V Assembly*

For the above assembly, we have the following machine code in the **instruction\_mem.mem**.

```
00f50513
01e58593
00060613
00068693
00170713
01f78793
02d61c63
40b508b3
00f8d8b3
00e8c8b3
00d89a63
00a68833
```

```
00b68533
010685b3
fed680e3
00d59663
00160613
fcd68ae3
40b50533
fcd686e3
00a688b3
01102023
00002903
```

*Listing 2. GCD RISC V Machine Code*

## Top Module

The top module of our design contains the complete datapath and controller as follows.

```
`include "Register_File.sv"
`include "Instruction_Memory.sv"
`include "Program_Counter.sv"
`include "Immediate_Generator.sv"
`include "ALU.sv"
`include "Branch_Condition.sv"
`include "Data_Memory.sv"
`include "Controller.sv"
`timescale 1ns/1ns

module top(
    input clk, rst
);

    wire[31:0] rdata1, rdata2;
    wire [31:0]
x0,x1,x2,x3,x4,x5,x6,x7,x8,x9,x10,x11,x12,x13,x14,x15,x16,x17,x18,x19,x20,x21
,x22,x23,x24,x25,x26,x27,x28,x29,x30,x31;
    wire [4:0] raddr1, raddr2, waddr;
    reg [31:0] wdata;
    wire [31:0] Instruction, PC, ALU_out, Immediate_Value, rdata;
    reg [31:0] A, B;
    wire [3:0] alu_op;
    wire [2:0] br_type;
    wire [1:0] wb_sel;
    wire sel_A, sel_B;

    Register_File rf(.rdata1(rdata1), .rdata2(rdata2),
        .x0(x0), .x1(x1), .x2(x2), .x3(x3), .x4(x4), .x5(x5), .x6(x6), .x7(x7),
        .x8(x8), .x9(x9), .x10(x10), .x11(x11), .x12(x12), .x13(x13), .x14(x14),
        .x15(x15), .x16(x16), .x17(x17), .x18(x18), .x19(x19), .x20(x20),
        .x21(x21), .x22(x22), .x23(x23), .x24(x24), .x25(x25), .x26(x26), .x27(x27),
        .x28(x28), .x29(x29), .x30(x30), .x31(x31),
        .raddr1(Instruction[19:15]), .raddr2(Instruction[24:20]),
```

```

.waddr(Instruction[11:7]), .wdata(wdata), .clk(clk), .rst(rst),
.reg_wr(reg_wr));

    Instruction_Memory im(.Instruction(Instruction), .Address(PC));

    Program_Counter pc(.ALU_out(ALU_out), .br_taken(br_taken), .clk(clk),
.rst(rst), .PC(PC));

    Immediate_Generator ig(.Immediate_Value(Immediate_Value),
.Instruction(Instruction), .unsign(unsign));

    always @(*) begin
        A <= sel_A ? PC : rdata1;
        B <= sel_B ? Immediate_Value : rdata2;
    end

    ALU al(.ALU_out(ALU_out), .A(A), .B(B), .alu_op(alu_op));

    Branch_Condition bcond(.br_taken(br_taken), .A(rdata1), .B(rdata2),
.br_type(br_type));

    Data_Memory dmem(.rdata(rdata), .wdata(rdata2), .addr(ALU_out),
        .wr_en(wr_en), .rd_en(rd_en), .clk(clk), .rst(rst));

    always_comb begin
        case (wb_sel)
            0 : wdata <= PC + 4;
            1 : wdata <= ALU_out;
            2 : wdata <= rdata;
        endcase
    end

    Controller cont(.Instruction(Instruction), .alu_op(alu_op),
.reg_wr(reg_wr), .sel_A(sel_A), .sel_B(sel_B),
        .wr_en(wr_en), .rd_en(rd_en), .br_type(br_type), .wb_sel(wb_sel),
.unsign(unsign));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
    end

endmodule

```

*Listing 3. Top Module Verilog*

For the top module, we have the following testbench.

```

@cocotb.test()
async def gcd_Test(dut):
    clk = Clock(dut.clk,10,"ns")
    cocotb.fork(clk.start())
    await RisingEdge(dut.clk)

```

*Listing 4. Top module testbench*

The timing diagram displays various digital signals over a 500 ns period. Key signals include:

- ALU\_out[31:0]:** Hexadecimal output values.
- A[31:0], B[31:0]:** Register outputs, mostly zero.
- e.Value[31:0]:** Hexadecimal value, mostly zero.
- ruction[31:0]:** Hexadecimal value, mostly zero.
- PC[31:0]:** Program Counter, mostly zero.
- alu\_op[3:0]:** ALU operation code, mostly zero.
- br\_taken:** Branch taken signal, mostly low.
- br\_type[2:0]:** Branch type, mostly 111.
- rd\_en:** Read enable, mostly low.
- rdata1[31:0], rdata2[31:0], rdata[31:0]:** Register data outputs, mostly zero.
- reg\_wr:** Register write enable, mostly low.
- rst:** Reset signal, mostly low.
- sel\_A, sel\_B:** Selection signals, mostly low.
- unsign:** Unsigned flag, mostly low.
- wb\_sel[1:0]:** Write back selection, mostly 00.
- wdata[31:0]:** Write data, mostly zero.
- wr\_en:** Write enable, mostly low.
- x0[31:0] through x23[31:0]:** Register inputs, mostly zero.

## Data Path

## Register File

```
module Register_File (
    output reg [31:0] rdata1, rdata2,
    output reg [31:0]
x0,x1,x2,x3,x4,x5,x6,x7,x8,x9,x10,x11,x12,x13,x14,x15,x16,x17,x18,x19,x20,x21
,x22,x23,x24,x25,x26,x27,x28,x29,x30,x31,
    input [4:0] raddr1, raddr2, waddr,
    input [31:0] wdata,
    input clk, rst, reg_wr
);

integer i;
reg [31:0] register_file [31:0];
always @(posedge clk) begin
    if(rst) begin
        for (i = 0; i <= 31; i=i+1) begin
            register_file[i] <= 0;
        end
    end else if(reg_wr) begin
```

```

        if(waddr != 0)
            register_file[waddr] <= wdata;
        end
    end

    always @(*) begin
        rdata1 <= register_file[raddr1];
        rdata2 <= register_file[raddr2];
        x1 <= register_file[0];
        x2 <= register_file[1];
        x3 <= register_file[3];
        x4 <= register_file[4];
        x5 <= register_file[5];
        x6 <= register_file[6];
        x7 <= register_file[7];
        x8 <= register_file[8];
        x9 <= register_file[9];
        x10 <= register_file[10];
        x11 <= register_file[11];
        x12 <= register_file[12];
        x13 <= register_file[13];
        x14 <= register_file[14];
        x15 <= register_file[15];
        x16 <= register_file[16];
        x17 <= register_file[17];
        x18 <= register_file[18];
        x19 <= register_file[19];
        x20 <= register_file[20];
        x21 <= register_file[21];
        x22 <= register_file[22];
        x23 <= register_file[23];
        x24 <= register_file[24];
        x25 <= register_file[25];
        x26 <= register_file[26];
        x27 <= register_file[27];
        x28 <= register_file[28];
        x29 <= register_file[29];
        x30 <= register_file[30];
        x31 <= register_file[31];
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
    end
end

```

*Listing 5. Register File verilog*

Using the following test bench for register file.

```

@cocotb.test()
async def Register_Test(dut):
    clk = Clock(dut.r1.clk, 10, "ns")
    cocotb.fork(clk.start())
    await RisingEdge(dut.r1.clk)
    dut.r1.rst <= 1
    await RisingEdge(dut.r1.clk)
    dut.r1.rst <= 0
    await RisingEdge(dut.r1.clk)

```


```

dut.r1.raddr1 <= 5
dut.r1.reg_wr <= 1
dut.r1.waddr <= 5
dut.r1.wdata <= 10
await RisingEdge(dut.r1.clk)
dut.r1.reg_wr <= 0
await RisingEdge(dut.r1.clk)

```

*Listing 6. Register File Testbench*

We get the following output waveform.

 

*Figure 3. Register File output*

## Instruction Memory

For instruction memory we have the following code.

```

module Instruction_Memory (
    output reg [31:0] Instruction,
    input [31:0] Address
);
    reg [31:0] instruction_memory [50:0];
    initial begin
        $readmemh("instruction_mem.mem", instruction_memory);
    end

    always @(*) begin
        Instruction <= instruction_memory[Address/4];
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
    end
endmodule

```

*Listing 7. Instruction Memory Verilog*



The instructions are being read from the instruction\_mem.mem file with following test contents.

```
00b58513
40b50533
00b55533
```

*Listing 8. Test Instructions*

We have the following testbench.

```
@cocotb.test()
async def Instruction_Test(dut):
    dut.i1.Address <= 8
    await Timer(2, 'ns')
    dut.i1.Address <= 4
    await Timer(2, 'ns')
    dut.i1.Address <= 0
    await Timer(2, 'ns')
```

*Listing 9. Instruction Memory Testbench*

We get the following output waveform



*Figure 4. Instruction Memory Output Waveform*

## Program Counter

For the program counter we have the following code.

```
module Program_Counter (
    input [31:0] ALU_out,
    input br_taken, clk, rst,
    output reg [31:0] PC
);
    always @(posedge clk) begin
        if(rst)
            PC <= 0;
        else
            PC <= br_taken ? ALU_out : PC + 4;
    end
endmodule
```

*Listing 10. Program Counter Verilog*

We have the following testbench.

```
@cocotb.test()
async def PC_Test(dut):
    clk = Clock(dut.p1.clk, 10, "ns")
    cocotb.fork(clk.start())
    await RisingEdge(dut.p1.clk)
    dut.p1.ALU_out <= 10
    dut.p1.br_taken <= 0
    dut.p1.rst <= 1
    await RisingEdge(dut.p1.clk)
    dut.p1.rst <= 0
    await RisingEdge(dut.p1.clk)
    for i in range(2): await RisingEdge(dut.p1.clk)
    dut.p1.br_taken <= 1
    await RisingEdge(dut.p1.clk)
```


```

dut.p1.br_taken <= 0
for i in range(2): await RisingEdge(dut.p1.clk)

```

*Listing 11. Program Counter Testbench*

We get the following output waveform.

 

*Figure 5. Program Counter Output Waveform*

## Immediate Generator

We have the following verilog code.

```

module Immediate_Generator (
    output reg [31:0] Immediate_Value,
    input [31:0] Instruction,
    input unsigned
);
    wire [6:0] opcode;
    assign opcode = Instruction[6:0];
    always_comb begin
        // Using Opcode
        case (opcode)
            // I Type Instruction
            7'd3, 7'd19, 7'd103: Immediate_Value <= unsigned ? {{20'b0},
Instruction[31:20]} : {{20{Instruction[31]}}, Instruction[31:20]};
            // S Type Instruction
            7'd35: Immediate_Value <= {{20{Instruction[31]}},
Instruction[31:25], Instruction[11:7]};
            // B Type Instruction
            7'd99: Immediate_Value <= {{20{Instruction[31]}}, Instruction[7],
Instruction[30:25], Instruction[11:8], 1'b0};
            // J Type Instruction
            7'd111: Immediate_Value <= {{12{Instruction[31]}},
Instruction[19:12], Instruction[20], Instruction[30:21], 1'b0};
            // U Type Instruction
            7'd23, 7'd55: Immediate_Value <= {Instruction[31:12], 12'b0};
            default: Immediate_Value <= 0;
        endcase
    end
endmodule

```

*Listing 12. Immediate Generator Verilog*

We have the following testbench.

```

@cocotb.test()
async def Imm_Gen(dut):
    # addi x10,x11,21
    dut.ig.Instruction <= 22381843
    await Timer(2,'ns')
    # sw x10,4(x0)
    dut.ig.Instruction <= 10494499
    await Timer(2,'ns')
    # beq x0,x0,-8
    dut.ig.Instruction <= 4261416163
    await Timer(2,'ns')
    # jal x0,-12

```


```

dut.ig.Instruction <= 4284477551
await Timer(2,'ns')
# lui x10,1234 = 5054464
dut.ig.Instruction <= 5055799
await Timer(2,'ns')

```

*Listing 13. Immediate Generator Testbench*

We get the following output waveform.

 

*Figure 6. Immediate Generator Waveform*

## ALU

Following is the ALU's verilog code.

```

module ALU (
    output reg [31:0] ALU_out,
    input [31:0] A, B,
    input [3:0] alu_op
);
    always_comb begin
        case(alu_op)
            0: ALU_out <= A + B; // addi
            1: ALU_out <= A << B; // slli
            2: ALU_out <= A ^ B; // xor
            3: ALU_out <= A >> B; // srli
            4: ALU_out <= A >>> B; // srai
            5: ALU_out <= A | B; // or
            6: ALU_out <= A & B; // and
            7: ALU_out <= A - B;
            8: ALU_out <= A;
            9: ALU_out <= B;
            default: ALU_out <= A + B;
        endcase
    end
endmodule

```

*Listing 14. ALU Verilog*

We have the following testbench.


```

@cocotb.test()
async def Instruction_Test(dut):
    dut.i1.Address <= 8
    await Timer(2,'ns')
    dut.i1.Address <= 4
    await Timer(2,'ns')
    dut.i1.Address <= 0
    await Timer(2,'ns')

```

*Listing 15. ALU Testbench*

We get the following output waveform.

 

*Figure 7. ALU Output*

## Branch and Jump Module

We have the following verilog code.

```
module Branch_Condition (
    output reg br_taken,
    input [31:0] A, B,
    input [2:0] br_type
);

    always_comb begin
        case (br_type)
            0: br_taken <= A == B;
            1: br_taken <= A != B;
            2: br_taken <= A < B;
            3: br_taken <= A > B;
            4: br_taken <= A <= B;
            5: br_taken <= A >= B;
            6: br_taken <= 1;
            default: br_taken <= 0;
        endcase
    end

endmodule
```


*Listing 16. Branch and Jump Verilog*

We have the following testbench.

```
@cocotb.test()
async def cond(dut):
    dut.bcond.A <= 10
    dut.bcond.B <= 10
    dut.bcond.br_type <= 0
    await Timer(2, 'ns')
    dut.bcond.br_type <= 1
    await Timer(2, 'ns')
    dut.bcond.br_type <= 6
    await Timer(2, 'ns')
```

*Listing 17. Branch and Jump Testbench*

We get the following output waveform.

 

*Figure 8. Branch and Jump Output Waveform*

## Data Memory

We have the following RTL.

```
module Data_Memory (
    output reg [31:0] rdata,
    input [31:0] wdata, addr,
    input wr_en, rd_en, clk, rst
);

    reg [8:0] data_mem [255:0];
    integer i;
```

```

always @(*) begin
    if(rd_en)
        rdata <=
{data_mem[addr],data_mem[addr+1],data_mem[addr+2],data_mem[addr+4]};
end

always @(posedge clk) begin
    if(rst) begin
        for(i=0;i<=255;i=i+1)
            data_mem[i] <= 0;
        end else begin
            if(wr_en)
                {data_mem[addr],data_mem[addr+1],data_mem[addr+2],data_mem[addr+4]}
<= wdata;
            end
        end
    end
end

```

*Listing 18. Data Memory Verilog*

We have the following testbench.


```

@cocotb.test()
async def Data_Test(dut):
    clk = Clock(dut.dmem.clk,10,"ns")
    cocotb.fork(clk.start())
    await RisingEdge(dut.dmem.clk)
    dut.dmem.rst <= 1
    await RisingEdge(dut.dmem.clk)
    dut.dmem.rst <= 0
    await RisingEdge(dut.dmem.clk)
    dut.dmem.addr <= 10
    dut.dmem.wdata <= 100
    dut.dmem.wr_en <= 1
    await RisingEdge(dut.rf.clk)
    dut.dmem.wr_en <= 0
    await RisingEdge(dut.rf.clk)
    dut.dmem.rd_en <= 1
    await RisingEdge(dut.rf.clk)
    dut.dmem.rd_en <= 0
    await RisingEdge(dut.rf.clk)

```

*Listing 19. Data Memory Testbench*

We get the following output waveform.

 

*Figure 9. Data Memory Output Waveform*

## Controller

For this datapath, all the RV32I instructions have been implemented except for **lb**, **lh**, **lbu**, **lhu**, **sb** and **sh**.

We have the following verilog code for our controller.

```

module Controller (
    input [31:0] Instruction,
    output reg [3:0] alu_op, output reg reg_wr, sel_A, sel_B,

```

```

    wr_en, rd_en, unsign, output reg [2:0] br_type, output reg [1:0] wb_sel
);
wire [6:0] opcode, func7 ;
wire [2:0] func3;
assign opcode = Instruction[6:0];
assign func7 = Instruction[31:25];
assign func3 = Instruction[14:12];
always_comb begin
    alu_op = 0;
    reg_wr = 0;
    sel_A = 0;
    sel_B = 0;
    wr_en = 0;
    rd_en = 0;
    wb_sel = 0;
    br_type = 3'b111;
    unsign = 0;
    case (opcode)
        // I type load
        7'd3: begin
            reg_wr = 1;
            sel_B = 1;
            rd_en = 1;
            wb_sel = 2;
        end
        // S type sw only
        7'd35: begin
            sel_B = 1;
            wr_en = 1;
            wb_sel = 2;
        end
        // I type
        7'd19: begin
            reg_wr = 1;
            sel_B = 1;
            rd_en = 1;
            wb_sel = 1;
            case (func3)
                7'd0: alu_op = 0;
                7'd1: begin
                    alu_op = 1;
                    unsign = 1;
                end
                7'd2: begin
                    alu_op = 10;
                end
                7'd3: begin
                    alu_op = 10;
                    unsign = 1;
                end
                7'd4: begin
                    alu_op = 2;
                end
                7'd5: begin
                    case (func7)
                        7'b0 : alu_op = 3;
                        7'b0100000: alu_op = 4;
                        default: alu_op = 3;
                    end
                end
            end
        end
    end
end

```

```

        endcase
    end
    7'd6: alu_op = 5;
    7'd7: alu_op = 6;
    default: alu_op = 0;
endcase
end
// U Type auipc
7'd23: begin
    alu_op = 0;
    sel_A = 1;
    sel_B = 1;
    br_type = 6;
end
// U Type lui
7'd55: begin
    alu_op = 9;
    reg_wr = 1;
    sel_B = 1;
    rd_en = 1;
    wb_sel = 1;
end
// R Type
7'd51: begin
    reg_wr = 1;
    rd_en = 1;
    wb_sel = 1;
    case (func3)
        7'd0: begin
            case (func7)
                7'b0: alu_op = 0;
                7'b0100000: alu_op = 7;
                default: alu_op = 0;
            endcase
        end
        7'd1: begin
            alu_op = 1;
        end
        7'd2: begin
            alu_op = 10;
        end
        7'd3: begin
            alu_op = 10;
            unsign = 1;
        end
        7'd4: begin
            alu_op = 2;
        end
        7'd5: begin
            case (func7)
                7'd0 : alu_op = 3;
                7'b0100000: alu_op = 4;
                default: alu_op = 3;
            endcase
        end
        7'd6: alu_op = 5;
        7'd7: alu_op = 6;
        default: alu_op = 0;
    endcase
end

```

```

        endcase
    end
    // B Type
    7'd99: begin
        sel_A = 1;
        sel_B = 1;
        case(func3)
            0: br_type = 0;
            1: br_type = 1;
            4: br_type = 2;
            5: br_type = 3;
            6: br_type = 4;
            7: br_type = 5;
        default: br_type = 7;
        endcase
    end
    // I JALR
    7'd103: begin
        sel_A = 1;
        sel_B = 1;
        wb_sel = 1;
        reg_wr = 1;
        br_type = 6;
    end
    // J Type
    7'd111: begin
        sel_A = 1;
        sel_B = 1;
        br_type = 6;
        reg_wr = 1;
        wb_sel = 0;
    end
    //default:
endcase
end
endmodule

```

*Listing 20. Control Unit Verilog*